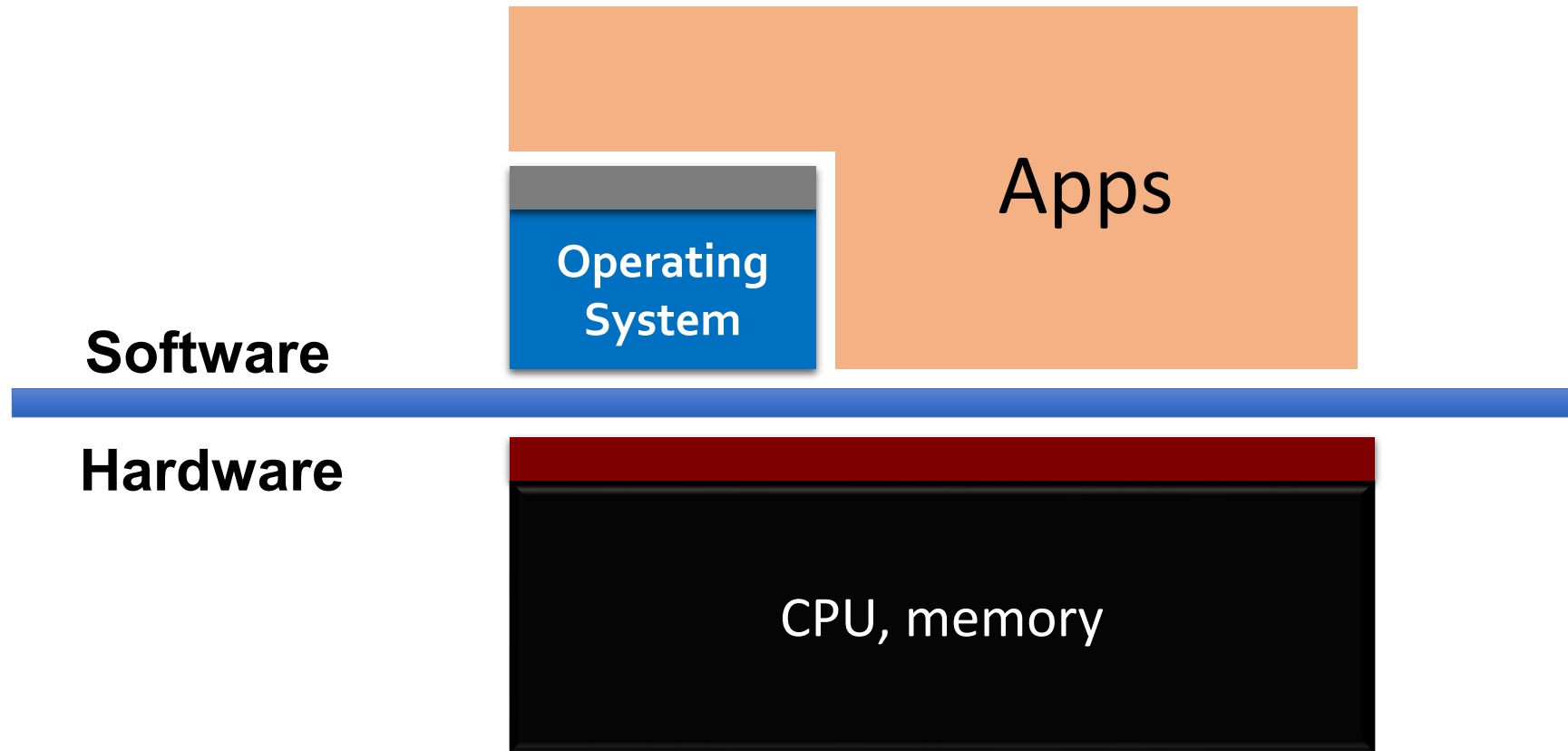


Architecture: Overview and Basic Logic Design

Jinyang Li

What we've learnt so far



What we've learnt so far

High level language program
(e.g. C)



Assembly program
(e.g. x86)



Machine language program
(e.g. x86)

Software

```
tmp = *a  
*a = *b  
*b = tmp
```

```
movq (%rdi), %rax  
movq (%rsi), %rbx  
movq %rbx, (%rdi)  
movq %rax, (%rsi)
```

```
1100110001010100110...
```

Hardware






Today's lecture plan

- Hardware Overview
 - CPU, memory, I/O devices
 - Moore's law
- Basics of Logic design

Computer hardware under the cover

Major components
of a computer

 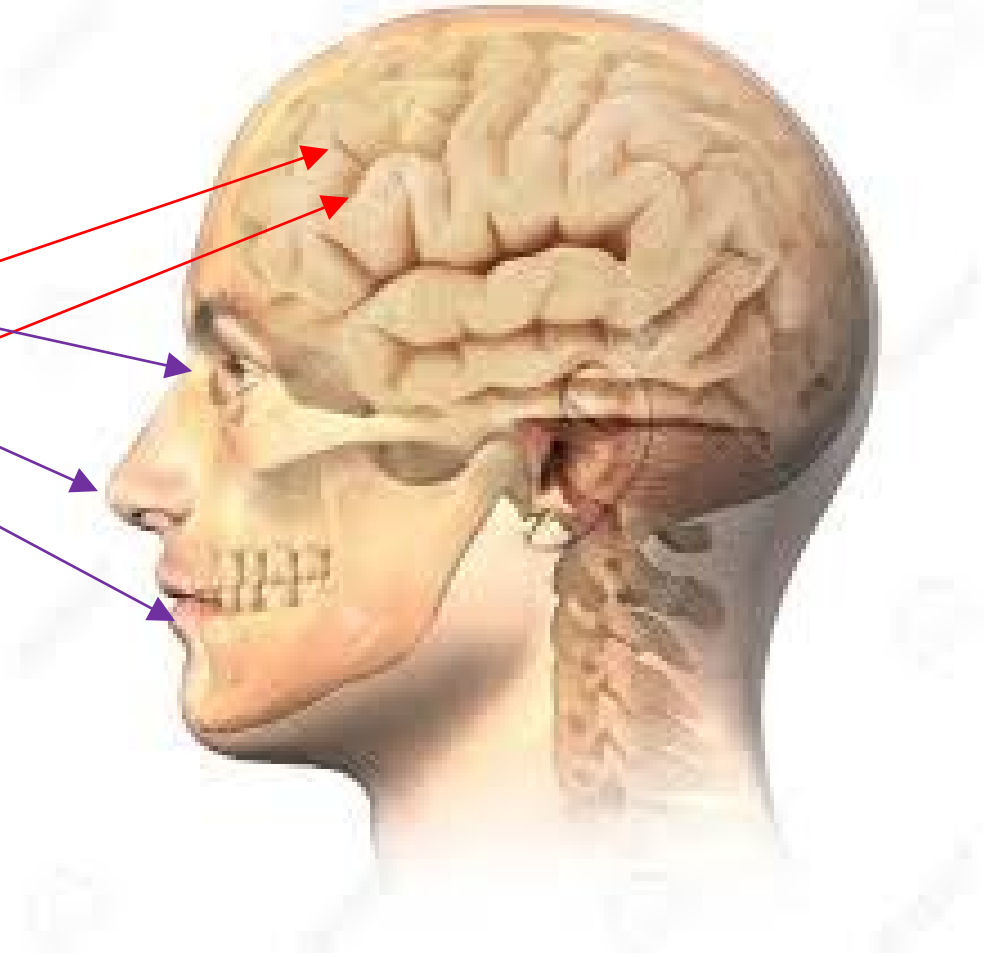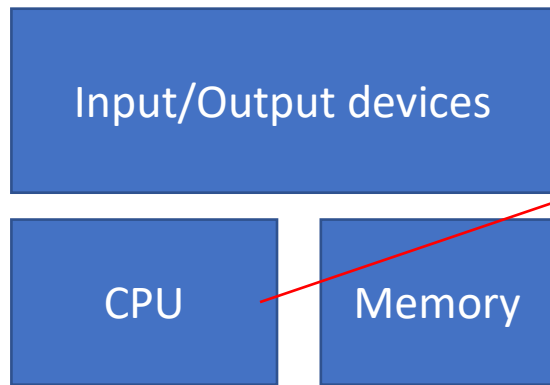

Computer hardware under the cover

Major components of a computer



rack-mountable server



Many racks full of rack-mountable servers
(data center)

Computer hardware under the cover

Major components of a computer

Input/Output devices

CPU

Memory



Network card



Solid state vs magnetic disk



LCD monitor (various brands)



16GB for \$100

 <p>AMD  (4)</p> <p>AMD EPYC 7501 32-Core 2.0 GHz (3.0 GHz Max Boost) Socket SP3 PS7501BEAFWOF Server Processor</p> <p>\$2,166 <small>(7 Offers)</small></p>	 <p>intel  (26)</p> <p>Intel Xeon E5-2680 v4 Broadwell-EP 2.4 GHz LGA 2011-3 120W BX80660E52680V4 Server Processor</p> <p><small>\$1,799.99</small></p> <p>See price in cart <small>(17 Offers)</small></p>
--	---

Teardown of a packaged computer



HP Pavilion Laptop - 15t touch

★★★★☆ 4.4 (245) [Write a review](#) | ENERGY STAR

Free shipping | Buy select PC and get an additional 20% off select HP accessory | 25% off Care Packs with select PC Purchase

[See similar products](#) >

- Windows 10 Home 64
- 8th Generation Intel® Core™ i7 processor
- Intel® UHD Graphics 620
- 8 GB memory; 1 TB HDD Storage; 16 GB Intel® Optane™ memory
- 15.6" diagonal HD touch display

[See all Specs](#)

Starting at ~~\$1,019.99~~
\$549.99 [Customize & buy](#)


Click to zoom



Teardown of a packaged computer



Teardown of a packaged computer

 

heat sink and cooling fan

If you peel away that fan....



Teardown of a packaged computer



Thermal paste makes the CPU hard to see



Intel® Core™ i7-5500U 3GHz processor

Teardown of a packaged computer



Micron 8GB memory



Teardown of a packaged computer



Hard-drive




Teardown of a packaged computer



Wireless card



We are in an exciting field

 

Why is CS a growth field?

Technological trend: exponential growth

An off/on switch controlled by electricity


Combine numerous transistors on a single chip

Year	Technology used in computers	Relative performance/unit cost
1951	Vacuum tube	1
1965	Transistor	35
1975	Integrated circuit	900
1995	Very large-scale integrated circuit	2,400,000
2013	Ultra large-scale integrated circuit	250,000,000,000


CSO will focus on CPU and memory

Moore's Law in CPU

 Moore's Law:
Transistor count
doubles every 2 years



Moore's Law in memory

 


Today's lecture plan

- Hardware Overview
 - CPU, memory, I/O devices
 - Moore's law
- Basics of Logic design


Digital Computer

 - Operate with only two voltage levels: high/low
 - that's why computers work with binary numbers
- The clock signal
 - “heartbeat” of the system




Digital Signals


x_3 x_2 x_1 x_0
↓ ↓ ↓ ↓

 


Digital signals

 

 Basic element of implementation: switches



 Close switch (if A is “1” or asserted)
→ light bulb is on (Z)




Open switch (if A is “0” or unasserted)
→ light bulb is off (Z)


$$\mathbf{Z} \equiv \mathbf{A}$$

Basic element of implementation: switches

 - Compose switches into more complex ones (Boolean functions):



$$Z \equiv A \text{ and B}$$

 

$$Z \equiv A \text{ or B}$$

Modern digital systems are done in CMOS transistors

Transistors act as switches

- Modern digital systems are implemented using CMOS transistors
- MOS transistors act as voltage-controlled switches



Bardeen, Shockley and Brattain at Bell Labs, 1948

Historical Note

- Early computer are built from ad hoc circuits
- Common patterns emerge: ANDs, ORs, ...
- Claude Shannon made the link to work of 19th century mathematician George Boole
 - Called it “Boolean” in his honor






Shannon





Boole

Gates: building blocks made from small groups of transistors

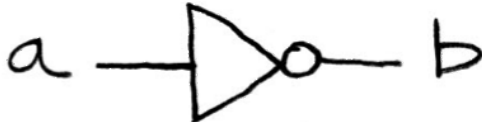			ab	c
AND			00	0
			01	0
			10	0
			11	1
			ab	c
OR			00	0
			01	1
			10	1
			11	1
			a	b
NOT			0	1
			1	0

More gates

  

Boolean Algebra

- Express (logic) functions with (logic) equations
 - $A \cdot B$ (AND), $A+B$ (OR), \bar{A} (NOT)

- Laws of Boolean algebra:

- Basic: $A+0=A$ $A+1=1$ $A \cdot 0=0$ $A \cdot 1=A$

- Inverse: $A+\bar{A}=1$ $A \cdot \bar{A}=0$ $\overline{A+B}=\bar{A} \cdot \bar{B}$ $\overline{A \cdot B}=\bar{A}+\bar{B}$

- Commutativity: $A+B=B+A$ $A \cdot B=B \cdot A$

- Associativity: $A+(B+C)=(A+B)+C$ $A \cdot (B \cdot C)=(A \cdot B) \cdot C$

- Distribution: $A \cdot (B+C)=A \cdot B+A \cdot C$ $A+(B \cdot C)=(A+B) \cdot (A+C)$

Boolean Algebra

$$A\bar{B} + \bar{A}$$

~~?~~
•

$$\bar{B} + \bar{A}B$$

Boolean Algebra

$$A\bar{B} + \bar{A} \neq \bar{B} + \bar{A}B$$

Method 1: Compare Truth Table

A	B	$A\bar{B} + \bar{A}$	$\bar{B} + \bar{A}B$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0


Boolean Algebra

$$A\bar{B} + \bar{A} \neq \bar{B} + \bar{A}B$$

Method 2: Simplify using basic laws

$$\begin{aligned} A\bar{B} + \bar{A} &= A\bar{B} + \bar{A} \cdot 1 = A\bar{B} + \bar{A} \cdot (B + \bar{B}) \\ &= \underbrace{A\bar{B} + \bar{A}B + \bar{A}\bar{B}} \\ &= (A + \bar{A})\bar{B} + \bar{A}B \\ &= \bar{B} + \bar{A} \cdot B \end{aligned}$$


Logic circuits == Boolean algebra

 

What is the Boolean expression?

$$A\bar{B} + \bar{A}$$

Logic circuits == Boolean algebra

 


What is the Boolean expression?


$$\bar{A}B + \bar{B}$$

Two types of logic circuit

 - Combinatorial circuit
 - output is dependent only on the input
- Sequential circuit
 - output is dependent on both input and state (memory)



Clock cycle:

 

How to implement any CL

- Implement a function with AND/OR/NOT


E.g.: Count # of 1's in 3-bit inputs

Step1: obtain truth tables

How to implement any CL

- Implement a function with AND/OR/NOT


E.g.: Count # of 1's in 3-bit inputs

 

How to implement any CL

- Implement a function with AND/OR/NOT

E.g.: Count # of 1's in 3-bit inputs

 

How to implement any CL

- Implement a function with AND/OR/NOT

E.g.: Count # of 1's in 3-bit inputs

Step 1: Write truth table

A	B	C	out ₁	out ₀
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

How to implement any CL

- Implement a function with AND/OR/NOT


E.g.: Count # of 1's in 3-bit inputs

Step 2: Find sum of product

A	B	C	out ₁
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{out}_1 = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

How to implement any CL

 

$$out_1 = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

How to implement any CL


- Implement a function with AND/OR/NOT

E.g.: Count # of 1's in 3-bit inputs

Step 2: Find sum of product


A	B	C	out ₀
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

How to implement any CL

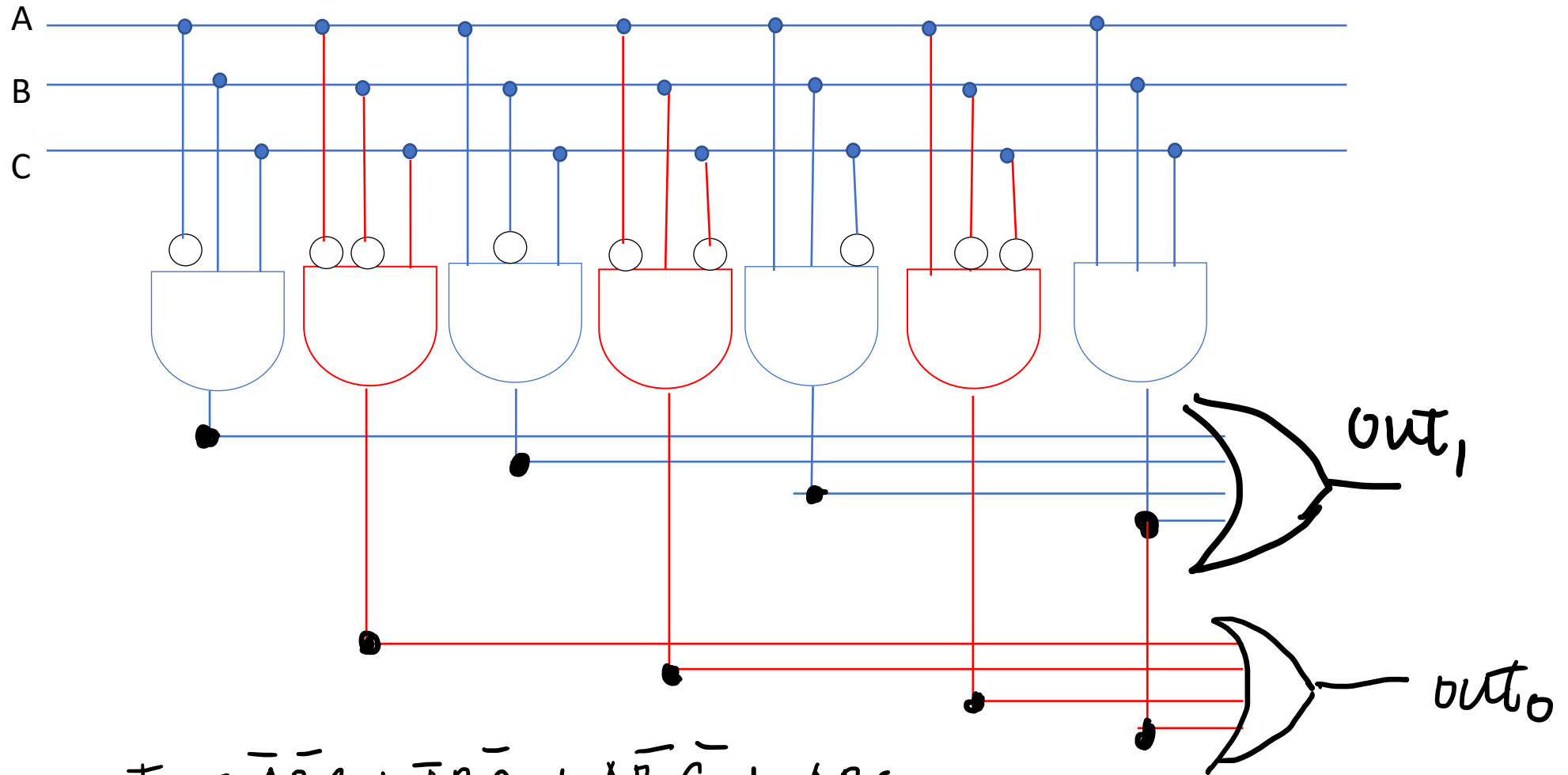


$$out_0 = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

PLA (Programmable Logic Array)


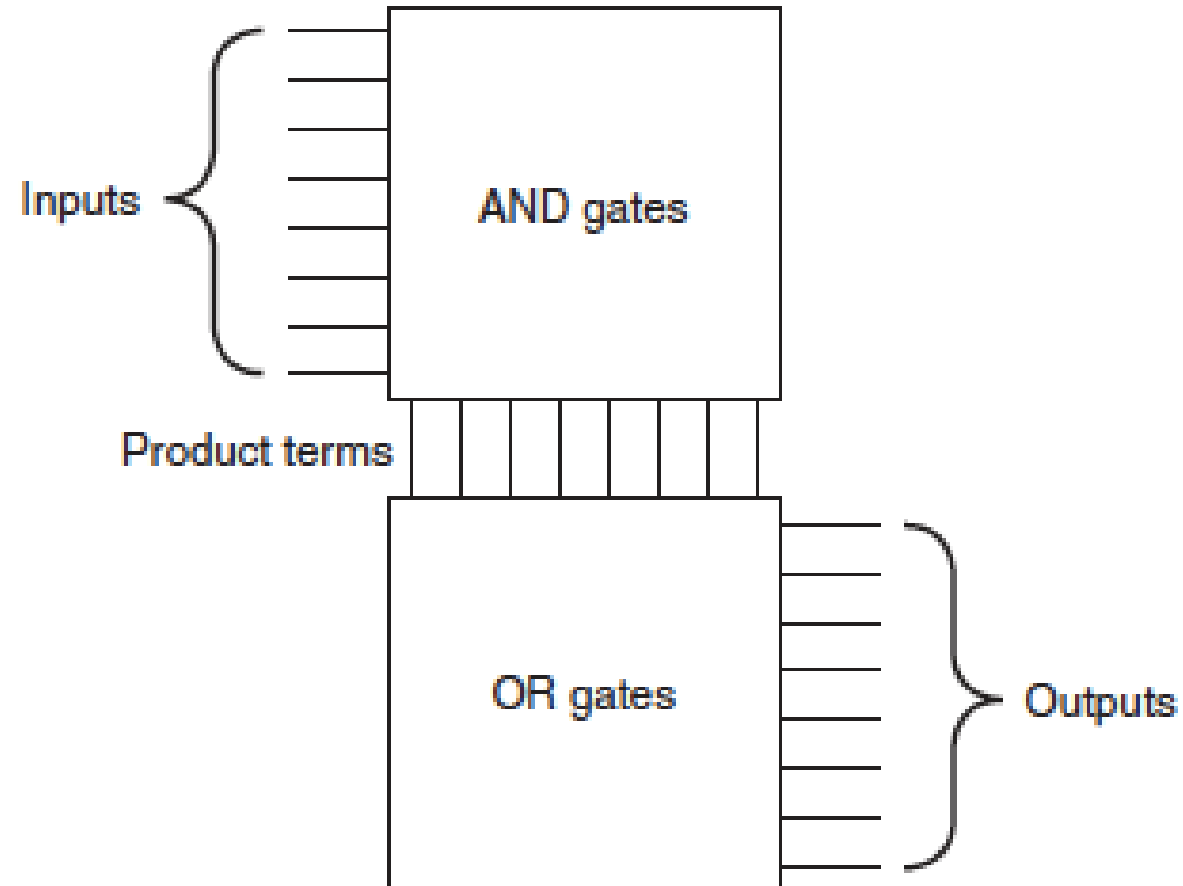


Common CL: decoder

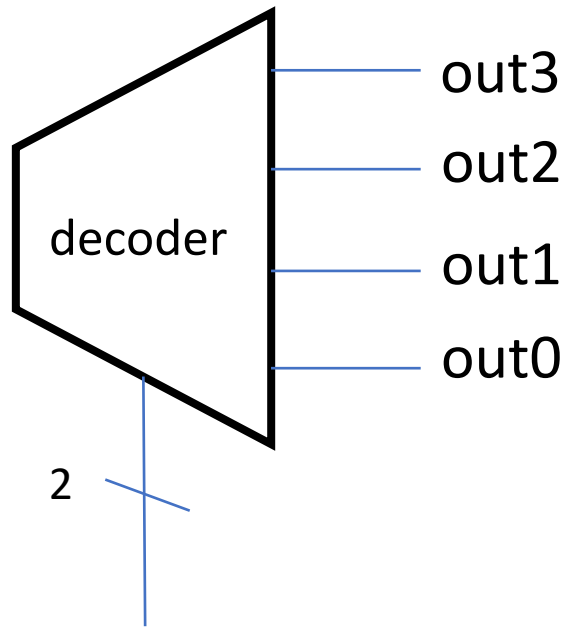


a1	a0	out3	out2	out1	out0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Common CL: decoder

  

Common CL: Multiplexor

 - Select among a set of inputs based on control



s1	s0	in3	in2	in1	in0	out
0	0	x	x	x	0	0
0	0	x	x	x	1	1
0	1	x	x	0	x	0
0	1	x	x	1	x	1
1	0	x	0	x	x	0
1	0	x	1	x	x	1
1	1	0	x	x	x	0
1	1	1	x	x	x	1

Common CL: Multiplexor

- Select among a set of inputs based on control

